

EE-363 Power Electronics

Assignment # 4

Spring 2022

Due Date: 11th June ,2022

Question 1

Derive impedance transformation of buck converter.

Question 2

Describe common components or necessary steps between buck and boost converter to make buck boost converter

Question 3

Take ups readings and give remarks.