

RAFAY AAMIR GULL

BSEE19047

POWER ELECTRONICS A3

For R load only	Single Phase Half Wave Rectifier	Single Phase Center Tap Full Wave Rectifier	Single Phase Full Wave Rectifier	Six Phase Star Rectifier	Three Phase Bridge Rectifier
Circuit Diagram					
Voltage and Current waveforms of Diode and load					
VDC , IDC and PDC	$V_{dc} = \frac{V_m}{2\pi} (1 - \cos(\omega t))$ $I = \frac{V_{dc}}{R} \quad P_{dc} = V_{dc} I_{dc}$	$V_{dc} = 0.6366 V_m$ $I = \frac{V_{dc}}{R} \quad P_{dc} = V_{dc} I_{dc}$	$V_{oc} = .637 V_{max.}$ $I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_s(t) d(\omega t) \quad P_{dc} = V_{dc} I_{dc}$	$V_{dc} = V_m \frac{q}{\pi} \sin\left(\frac{\pi}{q}\right)$ $I = \frac{V_{dc}}{R} \quad P_{dc} = V_{dc} I_{dc}$	$V_{dc} = 1.654 V_m$ $I = \frac{\sqrt{3} V_m}{R} \quad P_{dc} = V_{dc} I_{dc}$

Vrms , Irms and Prms	$V_{rms} = \frac{V_m}{2}$ $I_{rms} = \frac{I_m}{2}$ $Prms = (V_{rms})(I_{rms})$	$\frac{V_m}{\sqrt{2}}$ $I_{rms} = \frac{V_{rms}}{R}$ $Prms = (V_{rms})(I_{rms})$	$V_{rms} = \frac{V_m}{\sqrt{2}}$ $I_{rms} = \frac{I_m}{2}$ $Prms = V_{rms} * I_{rms}$	$V_{rms} = V_m \sqrt{\frac{3}{\pi} \left(\frac{\pi}{6} + \frac{\sin(\frac{\pi}{3})}{2} \right)}$ $I_{rms} = \frac{V_{rms}}{R}$ $Prms = V_{rms} * I_{rms}$	$V_{rms} = 1.6554 V_m$ $I_{rms} = 1.6554 V_m / R$ $Prms = V_{rms} * I_{rms}$
Efficiency	$\eta = \frac{P_{dc}}{P_{ac}}$	$\eta = (0.6366 V_m)^2 / (0.707 V_m)^2$	$\eta = \frac{P_{dc}}{P_{ac}}$	$\eta = \frac{P_{dc}}{P_{ac}}$	$\eta = (0.6366 V_m)^2 / (0.707 V_m)^2$
Form Factor (FF)	$Form\ Factor = \frac{V_{rms}}{V_{avg}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = 1.57$	$FF = 0.707 V_m / 0.6366 V_m$	$FF = I_{rms} / I_{avg}$	$FF = 0.707 V_m / 0.6366 V_m$	$FF = 0.707 V_m / 0.6366 V_m$
Ripple Factor (RF)	$RF = \sqrt{FF^2 - 1} = 1.21$	$RF = \sqrt{FF^2 - 1}$	$RF = \sqrt{FF^2 - 1}$	$RF = \sqrt{FF^2 - 1}$	$RF = \sqrt{FF^2 - 1}$
Total Harmonic Distortion (THD)	$THD = \frac{1}{V_{o1}} \left(\sum_{n=2,3,\dots}^{\infty} V_{on}^2 \right)^{1/2}$	$HF = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2} \right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$	$HF = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2} \right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$	$HF = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2} \right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$	$HF = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2} \right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$
Power Factor (PF)	$PF < 1$	$PF = \frac{P_{ac}}{VA}$	$P / (V_{rms} * I_{rms})$	$PF = P_{ac} / 3 V_{s1s}$	$PF = P_{ac} / 3 V_{s1s}$
Peak Inverse Voltage	$PIV = V_m = \sqrt{2} V_{rms}$	$PIV = 2 V_m.$	$V_{rms} = \frac{V_m}{\sqrt{2}}$	$\sqrt{3} V_m$	$\sqrt{3} V_m$
Output Voltage ripple frequency	150 Hz	120 Hz $0.637 V_{max}$	$6f$ <p>(where f is the frequency of AC supply)</p>	$0.637 V_{max}$	$0.637 V_{max}$